

# Module 5: Feedback Amplifiers and Stability

Welcome to this enhanced and comprehensive edition of Module 5: Feedback Amplifiers and Stability. In this module, we will embark on an even deeper exploration of feedback, an indispensable concept in electronics engineering. We will systematically dissect the principles of both positive and negative feedback, meticulously examining their operational mechanisms, the profound advantages they offer, and the inherent disadvantages they present. Our journey will then lead us through an exhaustive study of the four fundamental feedback topologies, elucidating how each configuration uniquely influences an amplifier's key characteristics, particularly its input and output impedances. We will rigorously quantify the impact of feedback on critical performance parameters such as gain, bandwidth, input resistance, output resistance, and distortion, grounding our understanding with practical calculations and numerical examples. The latter half of the module is dedicated to the paramount topic of amplifier stability, where we will uncover the conditions that lead to undesirable oscillations, understand the concept of conditional stability, and gain a qualitative yet insightful grasp of the Nyquist Stability Criterion. Finally, we will master the essential quantitative tools—Gain Margin and Phase Margin—crucial for robust feedback amplifier design, underscoring their importance in achieving predictable and reliable circuit performance. Every concept will be presented with clarity, supported by relevant formulas, and reinforced with practical numerical illustrations, ensuring a thorough and self-contained learning experience.

## 5.1 Concept of Feedback: Positive and Negative Feedback, Advantages and Disadvantages

At its most fundamental level, **feedback** in an electronic system is the process of extracting a portion of the output signal and returning it to the input, where it combines with the original input signal. This seemingly simple closed-loop interaction forms the backbone of countless sophisticated electronic circuits, enabling precise control, enhanced performance, and sometimes, intentional signal generation.

The core components that constitute a general feedback system are:

- **Basic Amplifier (Forward Path):** This is the primary amplification stage, possessing an open-loop gain, typically denoted by  $A$ . Its function is to amplify the effective input signal.
- **Feedback Network (Feedback Path):** This circuit samples a specific characteristic of the output signal (e.g., voltage or current) and transforms it into a form suitable for injection back into the input summing junction. This network is generally composed of passive components (resistors, capacitors, inductors) to ensure its stability and predictability. The feedback factor,  $\beta_F$ , represents the fraction or characteristic of the output signal that is returned to the input.

- **Summing/Comparison Network:** This is the point where the original input signal and the feedback signal are combined. The nature of this combination (addition or subtraction) dictates whether the feedback is positive or negative.
- **Load:** The external circuit or component connected to the amplifier's output, which the amplifier is designed to drive.

The efficacy and behavior of a feedback system are critically determined by how the feedback signal relates in phase to the original input signal at the summing junction.

## Positive Feedback (Regenerative Feedback)

**Positive feedback** occurs when the feedback signal, upon returning to the input, is in phase with (or adds to) the original input signal. This means the feedback actively reinforces the input, leading to a cumulative effect.

- **Mechanism of Operation:** Consider a small initial change in the input signal. This change is amplified by the basic amplifier, producing a corresponding change at the output. With positive feedback, a portion of this output change is fed back to the input in such a way that it *augments* the original input change. This amplified-and-reinforced signal then passes through the amplifier again, leading to an even larger output, which in turn leads to an even stronger feedback signal, and so on. This creates a self-reinforcing, "runaway" effect.
- **Fundamental Gain Equation (for Positive Feedback):** The closed-loop gain  $A_f$  for a positive feedback system is given by:  

$$A_f = \frac{A}{1 - A\beta F}$$
Where:
  - $A_f$  is the closed-loop gain (gain with feedback).
  - $A$  is the open-loop gain (gain without feedback).
  - $\beta F$  is the feedback factor, representing the ratio of the feedback signal to the output signal.
- **Critical Instability Condition:** A key observation from this formula is what happens when the term  $A\beta F$  approaches 1. As  $A\beta F \rightarrow 1$ , the denominator ( $1 - A\beta F$ ) approaches zero. Mathematically, this causes the closed-loop gain  $A_f$  to approach infinity. In a practical circuit, this signifies that the amplifier can produce an output signal even without any external input, meaning it will spontaneously generate oscillations. This is the basis for oscillator circuits. If  $A\beta F > 1$ , the system becomes unstable and the output will rapidly drive towards the power supply rails (saturate).
- **Advantages of Positive Feedback:**
  - **Oscillation Generation:** The most significant and widely utilized application of positive feedback is in the design of **oscillators**. By carefully satisfying the Barkhausen criterion (which we will discuss later), positive feedback allows for the generation of continuous, periodic waveforms (like sine waves, square waves, etc.) without the need for an external input signal.
  - **Increased Gain (Highly Sensitive Systems):** While typically avoided in amplifiers, positive feedback can theoretically lead to extremely high gain. This sensitivity can be exploited in certain specialized applications like Schmitt triggers for hysteresis, or in regenerative receivers for very weak signal detection, though these often toe the line of controlled instability.

- **Improved Selectivity (Q-enhancement):** In resonant circuits (like tuned amplifiers), positive feedback can effectively increase the Q-factor (quality factor) of the circuit, leading to a sharper and more selective frequency response. This means the circuit becomes highly sensitive to signals at the resonant frequency while significantly attenuating others.
- **Disadvantages of Positive Feedback:**
  - **Instability (Uncontrolled Oscillation):** This is the primary and most problematic disadvantage when positive feedback is unintentional in an amplifier. Even minute, unavoidable positive feedback paths can cause an amplifier designed for linear amplification to break into unwanted oscillations, making it unusable for its intended purpose.
  - **Increased Distortion:** Any non-linearity or distortion present in the amplifier's output is reinforced by positive feedback, leading to a degraded signal quality.
  - **Reduced Bandwidth:** Positive feedback tends to narrow the amplifier's operating frequency range, making it less versatile.
  - **Sensitivity to Parameter Variations:** Systems employing positive feedback are often highly sensitive to changes in component values or operating conditions, which can easily push them into or out of oscillation.

## Negative Feedback (Degenerative Feedback)

**Negative feedback** occurs when the feedback signal, upon returning to the input, is 180 degrees out of phase with (or subtracts from) the original input signal. This means the feedback actively opposes or counteracts the input, leading to a stabilizing and self-correcting effect.

- **Mechanism of Operation:** Consider an increase in the input signal. This is amplified, causing an increase at the output. With negative feedback, a portion of this increased output is fed back to the input in such a way that it *reduces* the effective input signal. This counteracts the initial increase, preventing the output from growing uncontrollably and forcing it to settle to a stable, amplified value that is less sensitive to variations. This forms a crucial self-regulation mechanism.
- **Fundamental Gain Equation (for Negative Feedback):** The closed-loop gain  $A_f$  for a negative feedback system is given by:

$$A_f = \frac{A}{1 + A\beta F}$$

Where  $A_f$ ,  $A$ , and  $\beta F$  are as defined previously.

**Key Insight:** Since the denominator is  $(1 + A\beta F)$ , and assuming  $A$  and  $\beta F$  are positive (which is usually the case for negative feedback loops), the closed-loop gain  $A_f$  will always be less than the open-loop gain  $A$ . **Gain Stability:** If the open-loop gain  $A$  is very large such that the loop gain  $A\beta F \gg 1$ , then the equation simplifies significantly:

$$A_f \approx \frac{A}{A\beta F} = \frac{1}{\beta F}$$

This is an extremely powerful result: the closed-loop gain of the amplifier becomes primarily determined by the feedback network components (passive elements like resistors, which are highly stable and precise) rather than the inherent, often variable, characteristics of the active amplifier device. This is the fundamental reason why negative feedback is so widely adopted in high-performance electronics.

- **Advantages of Negative Feedback:**

- **Improved Gain Stability (Reduced Sensitivity to A):** As shown above, the closed-loop gain becomes robust against variations in the open-loop gain  $A$  (which can change due to temperature fluctuations, power supply drift, component aging, or manufacturing tolerances). This leads to much more predictable and repeatable amplifier performance.
- **Reduced Non-linear Distortion:** Any non-linearity introduced by the amplifier itself (e.g., clipping, harmonic distortion) results in unwanted components at the output. Negative feedback feeds these components back to the input out of phase, effectively canceling a significant portion of them and linearizing the amplifier's response.
- **Increased Bandwidth:** Negative feedback extends the useful operating frequency range of the amplifier. By sacrificing gain, we can achieve a wider frequency response while maintaining stability. The gain-bandwidth product often remains constant.
- **Reduced Noise:** Negative feedback can significantly reduce noise that is generated *within* the amplifier stages themselves. It cannot, however, reduce noise that is present at the amplifier's input.
- **Precisely Controlled Input and Output Impedances:** Negative feedback provides a powerful mechanism to tailor the input and output impedances of the amplifier to suit specific source and load requirements, which is essential for efficient power transfer and signal integrity.
- **Improved Linearity:** The overall transfer characteristic of the amplifier becomes more linear, meaning the output is a more faithful replica of the input over a wider dynamic range.
- **Disadvantages of Negative Feedback:**
  - **Reduced Overall Gain:** The most immediate and often compensated disadvantage. To achieve a desired closed-loop gain, the open-loop gain  $A$  must be significantly higher. This might necessitate using multiple amplification stages or higher-gain active devices.
  - **Potential for Instability (Phase Shift Issues):** While generally a stabilizing mechanism, negative feedback can *turn into* positive feedback at higher frequencies due to unavoidable phase shifts introduced by parasitic capacitances and component time constants within the amplifier and feedback network. If the total phase shift around the loop reaches 360 degrees (or 0 degrees relative to the input) *while* the loop gain  $A\beta F$  is still unity or greater, the amplifier will oscillate. This necessitates careful design and often **frequency compensation** to ensure stability.
  - **Increased Circuit Complexity:** Implementing feedback requires additional components (the feedback network), which adds to the circuit's complexity and component count.

### Summary Comparison Table: Positive vs. Negative Feedback

Feature	Positive Feedback	Negative Feedback
Feedback Polarity	In-phase (reinforcing)	Out-of-phase (opposing)

Effect on Gain	Increases (can lead to oscillations)	Decreases (stabilizes gain)
Effect on Stability	Leads to instability, used for oscillation	Improves stability, can lead to instability if poorly designed
Effect on Distortion	Increases, degrades signal purity	Decreases, improves signal purity
Effect on Bandwidth	Decreases	Increases
Effect on Impedance	Highly variable, often increases input and output	Precisely controllable
Primary Application	Oscillators, regenerative circuits, Schmitt triggers	Amplifiers (linear, stable, low distortion), control systems
Export to Sheets		

---

## 5.2 Feedback Topologies

The configuration of how the feedback signal is sampled from the output and subsequently mixed with the input signal defines the **feedback topology**. There are four fundamental topologies, each uniquely impacting the amplifier's input and output impedance characteristics. These topologies are systematically categorized based on two key decisions:

### 1. Output Sampling Method:

- **Voltage Sampling (Shunt):** A portion of the output voltage is sensed. This is achieved by connecting the feedback network in *parallel* (shunt) with the output load. Voltage sampling tends to *decrease* the output impedance.
- **Current Sampling (Series):** A portion of the output current is sensed. This is achieved by connecting the feedback network in *series* with the output load. Current sampling tends to *increase* the output impedance.

### 2. Input Mixing Method:

- **Series Mixing:** The feedback signal (a voltage) is added or subtracted *in series* with the input voltage source. Series mixing tends to *increase* the input impedance.
- **Shunt Mixing:** The feedback signal (a current) is added or subtracted *in parallel* (shunt) with the input current source. Shunt mixing tends to *decrease* the input impedance.

By combining these two choices, we arrive at the four distinct feedback topologies:

### 1. Voltage Series Feedback (Series-Shunt Feedback)

- **Naming Convention:** The first term refers to the input mixing (Series), the second to the output sampling (Shunt/Voltage).

- **Output Sampling: Voltage** is sampled. The feedback network is connected in **shunt (parallel)** across the output. This aims to keep the output voltage constant.
- **Input Mixing:** The feedback signal (a voltage) is connected in **series** with the input voltage source. This means the feedback voltage is subtracted from the input voltage.
- **Ideal Open-Loop Amplifier Type:** For efficient operation, the basic open-loop amplifier (A) in this configuration should ideally be a **Voltage Amplifier** (characterized by very high input impedance and very low output impedance).
- **Feedback Factor ( $\beta F$ ):** This is a dimensionless voltage ratio.  

$$\beta F = V_{out} / V_f$$
Where  $V_f$  is the feedback voltage and  $V_{out}$  is the output voltage.
- **Closed-Loop Gain Type:** Voltage Gain ( $A_{vf} = V_{out} / V_{in}$ ).
- **Effect on Impedances:**
  - **Input Impedance ( $Z_{inf}$ ): Increased.** Because the feedback voltage effectively reduces the voltage seen by the input (for a given applied voltage), less current is drawn from the source, leading to a higher apparent input impedance.  

$$Z_{inf} = Z_{in}(1 + A_v \beta F)$$
Where  $Z_{in}$  is the open-loop input impedance and  $A_v$  is the open-loop voltage gain.
  - **Output Impedance ( $Z_{outf}$ ): Decreased.** Since the feedback actively samples the output voltage and adjusts the input to counteract changes, the amplifier behaves more like an ideal voltage source, which has zero output impedance.  

$$Z_{outf} = Z_{out} / (1 + A_v \beta F)$$
Where  $Z_{out}$  is the open-loop output impedance.
- **Practical Application:** The **non-inverting operational amplifier configuration** (e.g., voltage follower, non-inverting amplifier) is the most prominent example of voltage series feedback.

## 2. Current Series Feedback (Series-Series Feedback)

- **Naming Convention:** Series input mixing, Series output sampling.
- **Output Sampling: Current** is sampled. The feedback network is connected in **series** with the output load. This aims to keep the output current constant.
- **Input Mixing:** The feedback signal (a voltage) is connected in **series** with the input voltage source.
- **Ideal Open-Loop Amplifier Type:** For this configuration, the basic open-loop amplifier (A) should ideally be a **Transconductance Amplifier** (characterized by high input impedance and high output impedance, converting an input voltage to an output current).
- **Feedback Factor ( $\beta F$ ):** This is a resistance, as it converts output current to feedback voltage.  

$$\beta F = I_{out} / V_f$$
- **Closed-Loop Gain Type:** Transconductance Gain ( $G_{mf} = I_{out} / V_{in}$ ).
- **Effect on Impedances:**
  - **Input Impedance ( $Z_{inf}$ ): Increased.** Similar to voltage series, series mixing at the input increases the effective input impedance.

$$Z_{inf}=Z_{in}(1+G_m\beta F)$$

Where  $G_m$  is the open-loop transconductance gain.

- **Output Impedance ( $Z_{outf}$ ): Increased.** Since the feedback actively samples the output current and adjusts the input to maintain it, the amplifier behaves more like an ideal current source, which has infinite output impedance.

$$Z_{outf}=Z_{out}(1+G_m\beta F)$$

- **Practical Application:** While less commonly seen as a standalone op-amp configuration, a **common-emitter amplifier with an unbypassed emitter resistor** demonstrates the principle of current series feedback. The voltage developed across the emitter resistor provides a negative feedback voltage in series with the input.

### 3. Voltage Shunt Feedback (Shunt-Shunt Feedback)

- **Naming Convention:** Shunt input mixing, Shunt output sampling.
- **Output Sampling: Voltage** is sampled. The feedback network is connected in **shunt (parallel)** across the output.
- **Input Mixing:** The feedback signal (a current) is connected in **shunt (parallel)** with the input current source. This means the feedback current is subtracted from the input current.
- **Ideal Open-Loop Amplifier Type:** The basic open-loop amplifier (A) should ideally be a **Transresistance Amplifier** (characterized by very low input impedance and very low output impedance, converting an input current to an output voltage).
- **Feedback Factor ( $\beta F$ ):** This is a conductance, as it converts output voltage to feedback current.  

$$\beta F = V_{out}/I_f$$
- **Closed-Loop Gain Type:** Transresistance Gain ( $R_{mf}=V_{out}/I_{in}$ ).
- **Effect on Impedances:**
  - **Input Impedance ( $Z_{inf}$ ): Decreased.** Because the feedback current flows in parallel with the input source, it effectively shunts some current away, making the apparent input impedance lower. This is desirable when the amplifier is driven by a current source.  

$$Z_{inf}=1/R_m\beta F Z_{in}$$
Where  $R_m$  is the open-loop transresistance gain.
  - **Output Impedance ( $Z_{outf}$ ): Decreased.** Similar to voltage series, voltage sampling at the output reduces the effective output impedance.  

$$Z_{outf}=1/R_m\beta F Z_{out}$$
- **Practical Application:** The **inverting operational amplifier configuration** is a prime example of voltage shunt feedback. The feedback resistor connects the output to the inverting input, which acts as a virtual ground, effectively a shunt input.

### 4. Current Shunt Feedback (Shunt-Series Feedback)

- **Naming Convention:** Shunt input mixing, Series output sampling.
- **Output Sampling: Current** is sampled. The feedback network is connected in **series** with the output load.
- **Input Mixing:** The feedback signal (a current) is connected in **shunt (parallel)** with the input current source.

- **Ideal Open-Loop Amplifier Type:** The basic open-loop amplifier (A) should ideally be a **Current Amplifier** (characterized by low input impedance and high output impedance, converting an input current to an output current).
- **Feedback Factor ( $\beta F$ ):** This is a dimensionless current ratio.  

$$\beta F = I_{out} / I_f$$
- **Closed-Loop Gain Type:** Current Gain ( $A_{if} = I_{out} / I_{in}$ ).
- **Effect on Impedances:**
  - **Input Impedance ( $Z_{inf}$ ): Decreased.** Similar to voltage shunt, shunt mixing at the input reduces the effective input impedance.  

$$Z_{inf} = 1 / (1 + A_i \beta F) Z_{in}$$
Where  $A_i$  is the open-loop current gain.
  - **Output Impedance ( $Z_{outf}$ ): Increased.** Similar to current series, current sampling at the output increases the effective output impedance.  

$$Z_{outf} = Z_{out} (1 + A_i \beta F)$$
- **Practical Application:** A **common-base amplifier with an input current source** can exhibit current shunt feedback characteristics, where the input current and a feedback current combine at the emitter, and the output current is sampled.

**Summary Table of Feedback Topologies and Their Impedance Effects:**

This table consolidates the impact of each topology on the key impedance parameters, which is a critical design consideration for matching sources and loads.

Feedback Topology	Output Sampled	Input Mixed	Ideal Open-Loop Amplifier Type	Effect on Input Impedance ( $Z_{inf}$ )	Effect on Output Impedance ( $Z_{outf}$ )
<b>Voltage Series</b>	Voltage	Series	Voltage Amplifier	Increases ( $Z_{in}(1+A\beta F)$ )	Decreases ( $Z_{out}/(1+A\beta F)$ )
<b>Current Series</b>	Current	Series	Transconductance Amplifier	Increases ( $Z_{in}(1+A\beta F)$ )	Increases ( $Z_{out}(1+A\beta F)$ )
<b>Voltage Shunt</b>	Voltage	Shunt	Transresistance Amplifier	Decreases ( $Z_{in}/(1+A\beta F)$ )	Decreases ( $Z_{out}/(1+A\beta F)$ )
<b>Current Shunt</b>	Current	Shunt	Current Amplifier	Decreases ( $Z_{in}/(1+A\beta F)$ )	Increases ( $Z_{out}(1+A\beta F)$ )

Export to Sheets

Understanding these impedance transformations is vital for proper circuit design, ensuring efficient power transfer and minimal signal loading.

### 5.3 Effect of Feedback: On Gain, Bandwidth, Input Resistance, Output Resistance, Distortion



Negative feedback, by its very nature of error correction, profoundly modifies the performance characteristics of an amplifier. The factor  $(1+A\beta F)$ , often referred to as the **desensitivity factor** or **amount of feedback**, quantifies the degree to which these parameters are affected. The larger this factor, the stronger the impact of feedback.

The cornerstone formula for the closed-loop gain with negative feedback is:

$$A_f = \frac{A}{1+A\beta F}$$

Let's now systematically quantify the effects of this feedback on various critical amplifier parameters.

## 1. Effect on Gain

- **Gain Reduction:** As clearly evident from the fundamental formula, for any positive  $A\beta F$ , the denominator  $(1+A\beta F)$  will be greater than 1. Consequently, the closed-loop gain  $A_f$  will always be **less than** the open-loop gain  $A$ . This reduction in gain is the direct consequence of the feedback loop actively opposing the input signal.
- **Gain Desensitization (Stability of Gain):** This is one of the most significant advantages of negative feedback. If the open-loop gain  $A$  is very large (a common characteristic of modern op-amps and high-gain discrete amplifiers), such that the loop gain  $A\beta F \gg 1$ , then the closed-loop gain formula approximates to:  

$$A_f \approx \frac{A}{A\beta F} = \frac{1}{\beta F}$$

This approximation reveals that the closed-loop gain becomes virtually independent of the amplifier's internal open-loop gain  $A$ . Instead, it is solely determined by the feedback factor  $\beta F$ , which is typically set by passive, stable, and precise components (like resistors in a voltage divider). This ensures that the overall amplifier gain remains highly stable despite variations in the active devices (e.g., transistors, op-amps) due to temperature, power supply fluctuations, aging, or manufacturing tolerances.

**Numerical Example: Gain Desensitization in Detail** Consider a high-gain amplifier with an initial open-loop voltage gain  $A=200,000$ . It is configured with negative feedback using a feedback factor  $\beta F=0.005$ .

1. **Calculate the initial closed-loop gain ( $A_f$ ):** First, calculate the loop gain:  
 $A\beta F = 200,000 \times 0.005 = 1000$ . Now, calculate  $A_f$ :  
 $A_f = \frac{A}{1+A\beta F} = \frac{200,000}{1+1000} = \frac{200,000}{1001} \approx 199.800$
2. **Scenario: Open-loop gain drops by 30%** Suppose the open-loop gain  $A$  drops significantly by 30% due to an increase in temperature, from 200,000 to 140,000. Let's find the new closed-loop gain ( $A_f'$ ). New loop gain:  $A'\beta F = 140,000 \times 0.005 = 700$ .  
 New  $A_f'$ :  
 $A_f' = \frac{A'}{1+A'\beta F} = \frac{140,000}{1+700} = \frac{140,000}{701} \approx 199.715$
3. **Compare the changes:**
  - Percentage change in open-loop gain:  
 $\frac{140,000 - 200,000}{200,000} \times 100\% = -30\%$
  - Percentage change in closed-loop gain:  
 $\frac{199.715 - 199.800}{199.800} \times 100\% \approx -0.0425\%$

4. This dramatic difference illustrates the power of negative feedback. A large 30% variation in the inherent amplifier gain results in only a minuscule 0.0425% change in the overall amplifier gain, demonstrating exceptional stability and predictability.

## 2. Effect on Bandwidth

Negative feedback has the beneficial effect of **increasing the bandwidth** of an amplifier.

- **Mechanism (Gain-Bandwidth Product):** For many amplifiers, especially those dominated by a single pole in their frequency response (like op-amps compensated for unity gain stability), the **gain-bandwidth product (GBP)** is approximately constant. This means that if you reduce the gain, the bandwidth must increase proportionally to maintain a constant product.
- **Formula:** The closed-loop bandwidth (BWf) is related to the open-loop bandwidth (BW) by:  
$$BW_f = BW(1 + A\beta F)$$

This formula shows that the bandwidth is extended by the same desensitivity factor that reduces the gain. This is a direct consequence of trading off gain for improved frequency response.

**Numerical Example: Bandwidth Extension** An open-loop amplifier has a low-frequency gain  $A=5000$  and a 3dB bandwidth  $BW=20$  kHz. It is configured with negative feedback where the feedback factor  $\beta F=0.02$ .

1. **Calculate the loop gain ( $A\beta F$ ):**  $A\beta F=5000 \times 0.02=100$ .
2. **Calculate the closed-loop bandwidth (BWf):**  
 $BW_f = BW(1 + A\beta F) = 20 \text{ kHz} \times (1 + 100) = 20 \text{ kHz} \times 101 = 2020 \text{ kHz} = 2.02 \text{ MHz}$

The bandwidth has significantly increased from 20 kHz to 2.02 MHz, demonstrating the dramatic improvement in frequency response offered by negative feedback.

## 3. Effect on Input Resistance ( $Z_{inf}$ )

The effect on input resistance depends on how the feedback signal is mixed at the input:

- **Series Mixing (Voltage Series and Current Series Topologies):**
  - **Effect:** Input resistance **increases**.
  - **Mechanism:** When the feedback signal (a voltage) is connected in series with the input, it effectively opposes the input voltage (for negative feedback). This means that for a given input current drawn from the source, a larger input voltage is required to produce it, making the amplifier appear to have a higher input impedance. The amplifier "looks" more like an open circuit to the source.
  - **Formula:**  
$$Z_{inf} = Z_{in}(1 + A\beta F)$$

This characteristic is highly desirable for voltage amplifiers, as it minimizes the loading effect on the signal source.
- **Shunt Mixing (Voltage Shunt and Current Shunt Topologies):**
  - **Effect:** Input resistance **decreases**.

- **Mechanism:** When the feedback signal (a current) is connected in parallel (shunt) with the input, it effectively shunts some of the input current from the source away from the amplifier's internal input. This means that for a given input voltage, more current is drawn from the source, making the amplifier appear to have a lower input impedance. The amplifier "looks" more like a short circuit to the source.
- **Formula:**  

$$Z_{inf} = 1 + A\beta F Z_{in}$$

This characteristic is desirable when the amplifier is driven by a current source, as current sources prefer a low input impedance (closer to a short circuit) to deliver maximum current.

#### 4. Effect on Output Resistance ( $Z_{outf}$ )

The effect on output resistance depends on how the feedback signal is sampled at the output:

- **Voltage Sampling (Voltage Series and Voltage Shunt Topologies):**
  - **Effect:** Output resistance **decreases**.
  - **Mechanism:** When the output voltage is sampled, the feedback loop attempts to keep the output voltage constant regardless of changes in the load current. If the load current increases, causing the output voltage to drop, the feedback senses this drop and adjusts the amplifier's input to compensate, effectively boosting the output voltage back up. This behavior mimics an ideal voltage source, which has zero output impedance.
  - **Formula:**  

$$Z_{outf} = 1 + A\beta F Z_{out}$$

This is a highly desirable feature for voltage amplifiers, ensuring a stable output voltage even with varying loads.
- **Current Sampling (Current Series and Current Shunt Topologies):**
  - **Effect:** Output resistance **increases**.
  - **Mechanism:** When the output current is sampled, the feedback loop attempts to keep the output current constant regardless of changes in the load voltage. If the load resistance changes, causing the output current to try to change, the feedback senses this and adjusts the amplifier's input to compensate, effectively forcing the output current back to its desired value. This behavior mimics an ideal current source, which has infinite output impedance.
  - **Formula:**  

$$Z_{outf} = Z_{out}(1 + A\beta F)$$

This is a highly desirable feature for current amplifiers, ensuring a stable output current even with varying loads.

#### 5. Effect on Distortion and Noise

Negative feedback offers a significant improvement in the quality of the amplified signal by **reducing both non-linear distortion and noise generated within the amplifier itself.**

- **Mechanism (Error Correction):**

- **Distortion:** Non-linear distortion occurs due to the inherent non-linearities of active devices (e.g., transistors). These non-linearities introduce unwanted harmonic components into the output signal. When negative feedback is applied, these distortion components, being part of the output signal, are fed back to the input. Because it's negative feedback, these distortion components are inverted in phase and effectively subtracted from the internally generated distortion, leading to a substantial cancellation.
- **Noise:** Similarly, noise generated within the amplifier stages (e.g., thermal noise from resistors, shot noise from transistors) appears at the output. This internal noise is also fed back to the input, out of phase, and effectively reduced by the feedback loop.
- **Formula for Distortion Reduction:**  
 $D_f = 1 + A\beta F D$   
 Where  $D_f$  is the distortion with feedback and  $D$  is the distortion without feedback.
- **Formula for Noise Reduction (Internal Noise):**  
 $N_f = 1 + A\beta F N$   
 Where  $N_f$  is the noise with feedback and  $N$  is the noise generated within the amplifier without feedback.
- **Important Limitation:** It's crucial to understand that negative feedback **cannot reduce noise that is already present at the amplifier's input**. It only acts on noise and distortion components that originate *within* the amplifier circuit itself, after the feedback loop's input summing junction. Therefore, it's always important to minimize noise at the very first stage of an amplifier.

**Numerical Example: Distortion and Noise Reduction** An audio amplifier has a total harmonic distortion (THD) of 2% ( $D=0.02$ ) without feedback and generates internal noise equivalent to 0.5 mV RMS ( $N=0.0005$  V). Its open-loop gain is  $A=10,000$ . It is used with a negative feedback factor  $\beta F=0.01$ .

1. **Calculate the desensitivity factor ( $1+A\beta F$ ):**  $1+A\beta F=1+(10,000 \times 0.01)=1+100=101$ .
2. **Calculate the distortion with feedback ( $D_f$ ):**  
 $D_f = 1 + A\beta F D = 101 \times 0.02 \approx 0.000198 = 0.0198\%$   
 The THD has been significantly reduced from 2% to approximately 0.02%, a dramatic improvement in signal fidelity.
3. **Calculate the noise with feedback ( $N_f$ ):**  
 $N_f = 1 + A\beta F N = 101 \times 0.0005 \text{ V} \approx 0.0000495 \text{ V} = 4.95 \mu\text{V}$   
 The internally generated noise has been reduced from 0.5 mV to about 4.95  $\mu\text{V}$ , making the output cleaner.

These comprehensive examples clearly demonstrate the multifaceted benefits of negative feedback in enhancing the performance and stability of electronic amplifiers, making them more predictable, linear, and robust.

---

## 5.4 Calculation with Practical Circuits: Analyzing Common Feedback Amplifier Configurations

To solidify our understanding, let's analyze the closed-loop gain of two of the most ubiquitous feedback amplifier configurations built around **operational amplifiers (op-amps)**. Op-amps are nearly ideal voltage amplifiers characterized by extremely high open-loop gain, high input impedance, and low output impedance, making them perfect candidates for exploiting the benefits of negative feedback. Our analysis will rely on the simplifying assumptions of an ideal op-amp.

### Recap of Ideal Op-Amp Assumptions (for Simplified Analysis):

- **Infinite Open-Loop Voltage Gain ( $A \rightarrow \infty$ ):** This implies that for any finite output voltage, the differential input voltage ( $V_{diff} = V_+ - V_-$ ) must be zero. This leads to the "virtual short" concept.
- **Infinite Input Impedance ( $Z_{in} \rightarrow \infty$ ):** No current flows into the input terminals of the op-amp.
- **Zero Output Impedance ( $Z_{out} \rightarrow 0$ ):** The op-amp can supply any required output current without its output voltage changing.
- **Zero Input Offset Voltage:**  $V_+ = V_-$ .
- **Zero Input Bias Currents:** No current flows into the input terminals.

## 1. Non-Inverting Amplifier (Voltage Series Feedback)

This configuration is a classic embodiment of **Voltage Series Feedback**, where the output voltage is sampled and a proportional voltage is fed back in series with the input.

- **Circuit Description:**
  - The input signal ( $V_{in}$ ) is applied directly to the non-inverting (+) input terminal of the op-amp.
  - A resistive feedback network, typically a voltage divider consisting of two resistors,  $R_f$  (feedback resistor) and  $R_g$  (resistor to ground), is connected from the output ( $V_{out}$ ) back to the inverting (-) input terminal.
- **Systematic Analysis Steps (using Ideal Op-Amp assumptions):**
  - **Virtual Short Principle ( $V_+ = V_-$ ):** Since the non-inverting input is connected directly to  $V_{in}$ , we have  $V_+ = V_{in}$ . Due to the ideal op-amp's infinite open-loop gain and the presence of negative feedback, a "virtual short" exists between the input terminals. Therefore, the voltage at the inverting input ( $V_-$ ) is virtually equal to the voltage at the non-inverting input ( $V_+$ ).  

$$V_- = V_+ = V_{in}$$
  - **Voltage Divider Action of Feedback Network:** The output voltage  $V_{out}$  is divided by the feedback network ( $R_f$  and  $R_g$ ). The voltage at the inverting input,  $V_-$ , is precisely the voltage across  $R_g$ . Using the voltage divider rule:  

$$V_- = V_{out} \times \frac{R_g}{R_g + R_f}$$
  - **Equating the Two Expressions for  $V_-$ :** We now have two expressions for  $V_-$ . Equating them allows us to establish the relationship between  $V_{out}$  and  $V_{in}$ :  

$$V_{in} = V_{out} \times \frac{R_g}{R_g + R_f}$$
  - **Deriving the Closed-Loop Gain ( $A_f = V_{out}/V_{in}$ ):** Rearrange the equation to solve for the ratio of  $V_{out}$  to  $V_{in}$ :  

$$A_f = \frac{V_{out}}{V_{in}} = \frac{R_g + R_f}{R_g}$$

This can be further simplified to:

$$A_f = 1 + R_g R_f$$

- **Identification of Feedback Factor ( $\beta F$ ):** In the context of the general feedback formula  $A_f = A/(1 + A\beta F)$ , for  $A \rightarrow \infty$ , we get  $A_f = 1/\beta F$ . Comparing this with our derived gain formula  $A_f = 1 + R_f/R_g$ , we can deduce the feedback factor:

$$\beta F = 1 + R_g R_f = R_g + R_f R_g$$

This matches the voltage divider ratio, confirming that the fraction of the output voltage fed back to the input is indeed  $R_g/(R_g + R_f)$ .

- **Key Characteristics:**
  - **Gain:** Always greater than or equal to 1. Cannot be less than 1.
  - **Input Impedance:** Extremely high (approaching infinity, like the ideal op-amp itself). It is increased by the desensitivity factor.
  - **Output Impedance:** Extremely low (approaching zero, like the ideal op-amp itself). It is decreased by the desensitivity factor.
  - **Phase Relationship:** Output is in phase with the input.

**Numerical Example: Non-Inverting Amplifier Calculation** An op-amp is configured as a non-inverting amplifier with  $R_f = 22 \text{ k}\Omega$  and  $R_g = 2 \text{ k}\Omega$ .

1. **Calculate the closed-loop gain ( $A_f$ ):**  
 $A_f = 1 + R_g R_f = 1 + 2 \text{ k}\Omega / 22 \text{ k}\Omega = 1 + 11 = 12$   
This amplifier will provide a precise voltage gain of 12.
2. **If  $V_{in} = 0.5 \text{ V}$  peak-to-peak, what is  $V_{out}$ ?**  
 $V_{out} = A_f \times V_{in} = 12 \times 0.5 \text{ V} = 6 \text{ V}$  peak-to-peak

## 2. Inverting Amplifier (Voltage Shunt Feedback)

This configuration is a prime example of **Voltage Shunt Feedback**, where the output voltage is sampled, and a proportional current is fed back in shunt (parallel) with the input.

- **Circuit Description:**
  - The non-inverting (+) input terminal of the op-amp is connected directly to ground.
  - The input signal ( $V_{in}$ ) is applied to the inverting (-) input terminal through an input resistor ( $R_{in}$ ).
  - A feedback resistor ( $R_f$ ) connects the output ( $V_{out}$ ) back to the inverting (-) input terminal.
- **Systematic Analysis Steps (using Ideal Op-Amp assumptions):**
  - **Virtual Ground Principle ( $V_- = V_+$ ):** Since the non-inverting input ( $V_+$ ) is connected to ground, we have  $V_+ = 0 \text{ V}$ . Due to the ideal op-amp's infinite open-loop gain and the presence of negative feedback, a "virtual short" exists between the input terminals. Therefore, the voltage at the inverting input ( $V_-$ ) is virtually at ground potential.  
 $V_- = V_+ = 0 \text{ V}$   
This point is often referred to as a "virtual ground."
  - **Input Current ( $I_{in}$ ):** The current flowing from the input source ( $V_{in}$ ) through  $R_{in}$  towards the virtual ground point ( $V_-$ ) can be calculated using Ohm's Law. Since the op-amp's input impedance is infinite, no current flows *into* the

inverting input terminal of the op-amp itself.

$$I_{in} = R_{in}V_{in} - V_- = R_{in}V_{in} - 0 = R_{in}V_{in}$$

- **Feedback Current ( $I_f$ ):** Because no current enters the op-amp's input, all the input current  $I_{in}$  must flow *through* the feedback resistor  $R_f$  towards the output.

$$I_f = I_{in}$$

- **Output Voltage ( $V_{out}$ ):** The output voltage is the voltage at the virtual ground ( $V_-$ ) minus the voltage drop across  $R_f$  due to the current  $I_f$  flowing through it. Note the direction of current flow (from virtual ground towards output for positive output voltage, or from output towards virtual ground for negative output voltage).

$$V_{out} = V_- - I_f R_f = 0 - I_{in} R_f$$

Substitute the expression for  $I_{in}$ :

$$V_{out} = -(R_{in}V_{in})R_f$$

- **Deriving the Closed-Loop Gain ( $A_f = V_{out}/V_{in}$ ):** Rearrange the equation to solve for the ratio of  $V_{out}$  to  $V_{in}$ :

$$A_f = V_{in}V_{out} = -R_{in}R_f$$

- **Key Characteristics:**

- **Gain:** Can be set to any desired value (positive or negative magnitude, but the sign is always negative).
- **Inversion:** The output signal is always 180 degrees out of phase with the input signal (indicated by the negative sign in the gain formula).
- **Input Impedance:** The input impedance is approximately equal to  $R_{in}$  (since the inverting input is a virtual ground). It is significantly decreased by the feedback.
- **Output Impedance:** Extremely low (approaching zero).

**Numerical Example: Inverting Amplifier Calculation** An op-amp is configured as an inverting amplifier with  $R_{in}=10\text{ k}\Omega$  and  $R_f=100\text{ k}\Omega$ .

1. **Calculate the closed-loop gain ( $A_f$ ):**

$$A_f = -R_{in}R_f = -10\text{ k}\Omega/100\text{ k}\Omega = -10$$

This amplifier will provide an inverting voltage gain of -10.

2. **If  $V_{in}=0.2\text{ V (DC)}$ , what is  $V_{out}$ ?**

$$V_{out} = A_f \times V_{in} = -10 \times 0.2\text{ V} = -2\text{ V}$$

### 3. Voltage Follower (Unity Gain Buffer)

A specialized but extremely important case of the non-inverting amplifier is the **Voltage Follower**, also known as a unity-gain buffer. It exemplifies **Voltage Series Feedback** in its simplest form.

- **Circuit Description:**

- The input signal ( $V_{in}$ ) is applied directly to the non-inverting (+) input terminal.
- The output ( $V_{out}$ ) is connected directly back to the inverting (-) input terminal. (This corresponds to setting  $R_f=0$  and  $R_g=\infty$  in the non-inverting amplifier formula, or effectively shorting the output to the inverting input).

- **Systematic Analysis Steps (using Ideal Op-Amp assumptions):**

- **Virtual Short Principle ( $V_+ = V_-$ ):** Since  $V_+ = V_{in}$ , then  $V_- = V_{in}$ .
- **Direct Feedback Connection:** The output  $V_{out}$  is directly connected to the inverting input  $V_-$ .  
 $V_{out} = V_-$
- **Deriving the Closed-Loop Gain ( $A_f = V_{out}/V_{in}$ ):** Substituting  $V_- = V_{in}$  into the previous equation:  
 $V_{out} = V_{in}$   
Therefore:  
 $A_f = V_{in}/V_{out} = 1$
- **Key Characteristics:**
  - **Unity Gain:** The output voltage precisely follows the input voltage, hence "voltage follower."
  - **Extremely High Input Impedance:** Makes it ideal for connecting to high-impedance sources (e.g., sensor outputs) without loading them.
  - **Extremely Low Output Impedance:** Makes it ideal for driving low-impedance loads (e.g., long cables, small speakers) without significant voltage drop or distortion.
- **Primary Application:** Its main purpose is **impedance buffering or isolation**. It provides no voltage gain but offers substantial current gain and power gain by transforming impedances. This prevents a high-impedance source from being loaded down by a low-impedance load, ensuring the signal integrity from the source.

**Numerical Example: Voltage Follower** If a signal from a microphone with an output impedance of 1 M $\Omega$  is connected to a power amplifier with an input impedance of 10 k $\Omega$  directly, the microphone's output voltage would be severely loaded and attenuated. However, if a voltage follower is placed between the microphone and the power amplifier:

- The voltage follower's extremely high input impedance (e.g., 10<sup>12</sup>  $\Omega$  for an op-amp) effectively "sees" the microphone as an ideal source, drawing negligible current.
- The voltage follower's extremely low output impedance (e.g., 1  $\Omega$  or less) can then efficiently drive the 10 k $\Omega$  input of the power amplifier without significant voltage drop. The output voltage of the voltage follower will be virtually identical to the microphone's input voltage, but with the ability to supply much more current.

By systematically applying the ideal op-amp rules and understanding the feedback topologies, we can readily analyze and predict the behavior of these fundamental and widely used amplifier configurations.

---

## 5.5 Concept of Stability in Feedback Amplifiers: Oscillations, Conditional Stability

While negative feedback is invaluable for its performance-enhancing qualities, it introduces a critical design challenge: the potential for **instability**. An otherwise functional amplifier can break into unwanted, self-sustaining oscillations if the feedback loop is not properly designed and controlled. Ensuring stability is paramount for any feedback amplifier.



## What is Stability?

An amplifier is considered **stable** if, following any transient disturbance (e.g., power-up, input signal change, a sudden load change), its output eventually settles to a predictable, steady-state value. This steady state could be zero volts (in the absence of an input) or a faithful, amplified replica of the input signal.

Conversely, an amplifier is **unstable** if, under certain conditions, its output spontaneously generates an uncontrolled, continuous alternating current (AC) signal without any external input, or if its output saturates and "latches up" against the power supply rails. This uncontrolled behavior is known as **oscillation**.

## Oscillations: The Barkhausen Criterion

Oscillations occur when the feedback intended to be negative effectively becomes positive feedback at a specific frequency, and the circuit provides enough gain at that frequency to sustain the oscillation. The conditions for sustained oscillations are formally described by the **Barkhausen Criterion**:

For a feedback system to oscillate, two conditions must be met simultaneously at the frequency of oscillation ( $f_o$ ):

1. **Loop Gain Magnitude Condition:** The magnitude of the loop gain,  $|A\beta F|$ , must be equal to or greater than unity (1).

$$|A\beta F| \geq 1$$

This condition implies that the signal going around the loop is not attenuated; it is either maintained or amplified.

2. **Phase Shift Condition (Phase Angle Condition):** The total phase shift around the feedback loop must be zero degrees ( $0^\circ$ ) or an integer multiple of 360 degrees ( $n \times 360^\circ$ ).

$$\angle(A\beta F) = 0^\circ \text{ or } n \times 360^\circ$$

In the context of negative feedback, this means that the signal, after traversing the amplifier and the feedback network, arrives back at the summing junction *in phase* with the initial input, effectively turning negative feedback into positive feedback at that specific frequency. Since negative feedback typically introduces an inherent 180-degree phase shift (for an inverting configuration) or assumes a 0-degree shift (for non-inverting), the additional phase shifts accumulating from reactive components (capacitors and inductors, both parasitic and intentional) must combine to cancel out this initial relationship, resulting in a net 0 or 360-degree loop phase shift.

- **How Negative Feedback Can Turn Positive:** Real-world amplifiers and their associated feedback networks are not ideal and introduce phase shifts that are dependent on frequency.
  - At low frequencies, a well-designed negative feedback amplifier maintains the desired phase relationship (e.g., a 180-degree phase shift for an inverting configuration, or an effective cancellation for a non-inverting one, resulting in negative feedback).

- As the operating frequency increases, parasitic capacitances (junction capacitances in transistors, stray capacitances between wires, internal op-amp compensation capacitors) and sometimes inductive effects begin to play a significant role. These reactive elements introduce additional phase shifts. Each RC low-pass filter stage, for instance, can contribute up to 90 degrees of phase lag at high frequencies.
- If an amplifier has multiple poles (frequency points where the gain starts to roll off at -20 dB/decade), these poles contribute cumulative phase lag. For example, a three-pole amplifier can provide up to 270 degrees of phase lag. If, at a certain frequency, this accumulated phase lag (say, 270 degrees) combined with the inherent 180-degree phase shift of the inverting amplifier (total 450 degrees, which is 90 degrees past 360 degrees, or 90 degrees relative to input in a non-inverting context) or whatever path the signal takes to eventually arrive 0 or 360 degree, and if at this exact frequency the loop gain  $|A\beta F|$  is still 1 or greater, then the Barkhausen criterion is met, and the amplifier will oscillate. The circuit begins to generate its own signal because any minute noise signal at that frequency gets amplified, fed back in phase, and re-amplified, building up exponentially until limited by power supply rails.

## Conditional Stability

An amplifier is said to be **conditionally stable** if it remains stable only as long as its open-loop gain ( $A$ ) stays within a specific range. If the open-loop gain drops below a certain minimum value (e.g., due to temperature increase or component aging), the amplifier might suddenly become unstable and oscillate.

- **Graphical Interpretation (from Bode Plot Perspective):** A conditionally stable amplifier's loop gain phase plot might cross -180 degrees at a frequency where the gain is greater than 0 dB (indicating instability), but then the phase plot might cross -180 degrees *again* at an even higher frequency where the gain is less than 0 dB (indicating stability at very high frequencies). This "crossing back" into stability at higher frequencies, only after an unstable region, defines conditional stability.
- **Practical Implications:** Conditionally stable designs are generally avoided in professional engineering. They are risky because a seemingly minor change in operating conditions or component characteristics (which inevitably occurs over time and temperature) could push the amplifier into an unstable state. Robust designs aim for **unconditional stability**, meaning the amplifier remains stable regardless of decreases in its open-loop gain.

## Factors Contributing to Instability

Understanding the sources of phase shift is crucial for preventing instability:

1. **Internal Parasitic Capacitances:** Every active device (transistor, diode) has inherent parasitic capacitances (e.g., collector-base capacitance, junction capacitance, diffusion capacitance). Similarly, all wiring and interconnections within a circuit exhibit stray capacitance. These capacitances form unintentional low-pass

filters with resistances, introducing poles into the transfer function, which cause phase lag at higher frequencies.

2. **Multiple Amplifier Stages:** In multistage amplifiers, each stage contributes its own phase shift. If these phase shifts accumulate, particularly at frequencies where the overall loop gain is still significant, the total phase shift can easily reach 180 degrees (or 360 degrees relative to total loop), leading to instability. For instance, a common op-amp structure might have three or more gain stages, each contributing a dominant pole.
3. **Feedback Network Reactive Components:** While usually designed with resistors for fixed  $\beta F$ , if capacitors or inductors are inadvertently (parasitics) or intentionally included in the feedback network, they will introduce additional frequency-dependent phase shifts, directly impacting stability.
4. **Load Characteristics:** The characteristics of the load connected to the amplifier's output can significantly affect its stability. A capacitive load, for example, forms a pole with the amplifier's output resistance, adding further phase lag and reducing the phase margin, potentially causing oscillations.
5. **Power Supply Decoupling:** Inadequate or improperly placed power supply decoupling capacitors can lead to power supply impedance rising at certain frequencies. This can create unintended feedback paths or cause internal amplifier nodes to interact in ways that lead to oscillations.
6. **Input Filtering:** While often beneficial for noise reduction, input filters can also introduce additional poles and phase shifts that must be accounted for in the overall loop stability analysis.

To combat instability and ensure reliable operation, circuit designers employ **frequency compensation** techniques. These methods strategically add capacitors (or sometimes resistor-capacitor networks) to the amplifier's internal stages or external feedback path. The primary goal of compensation is to deliberately shape the loop gain's frequency response, typically by introducing a dominant pole at a low frequency, ensuring that the loop gain drops below unity (0 dB) *before* the total phase shift around the loop reaches the critical 180 degrees (or 360 degrees for a conceptual positive feedback loop). This ensures sufficient gain and phase margins, which we will discuss next.

---

## 5.6 Nyquist Stability Criterion (Qualitative): Understanding the Basics

The **Nyquist Stability Criterion** is a powerful and general graphical method for analyzing the stability of linear feedback control systems, including feedback amplifiers. It provides a definitive answer to whether a system is stable, unstable, or conditionally stable by examining the frequency response of the open-loop transfer function (the loop gain,  $A\beta F$ ). While a rigorous mathematical treatment involves complex contour mapping in the s-plane, we will focus on a qualitative understanding using the common **Nyquist plot**.

### The Loop Gain: The Core of Stability Analysis

The critical parameter for stability analysis is the **loop gain**, which is the product of the open-loop amplifier gain  $A(s)$  and the feedback factor  $\beta_F(s)$ . Since both  $A$  and  $\beta_F$  are frequency-dependent (and thus complex numbers), the loop gain  $T(s)$  is also a complex function of frequency (or the complex variable 's' in general):  $T(s) = A(s) \beta_F(s)$ . For sinusoidal steady-state analysis, we replace 's' with  $j\omega$ :

$$T(j\omega) = A(j\omega) \beta_F(j\omega)$$

This function encapsulates both the magnitude and phase shift encountered by a signal as it travels once around the feedback loop.

## The Nyquist Plot (Qualitative Concept)

A **Nyquist plot** is a graphical representation of the complex loop gain  $T(j\omega)$  in the complex plane as the angular frequency  $\omega$  varies from 0 to positive infinity ( $\infty$ ). Each point on the plot corresponds to a specific frequency, where the distance from the origin represents the magnitude  $|T(j\omega)|$  and the angle with the positive real axis represents the phase angle  $\angle T(j\omega)$ .

- **The Critical Point (-1, 0):** The **Nyquist Stability Criterion** revolves around a specific point in the complex plane: the point with coordinates  $(-1, 0)$ , which corresponds to a magnitude of 1 and a phase angle of -180 degrees (or 180 degrees). This point is often called the **critical point** or **Nyquist point**.
  - Recall the Barkhausen criterion for oscillation:  $|A\beta_F| \geq 1$  and  $\angle(A\beta_F) = 0^\circ$  or  $360^\circ$ . For negative feedback, if the inherent 180-degree phase shift is turned into 0 or 360 degrees by additional phase shifts, this corresponds to the loop gain  $A\beta_F$  having a phase of  $\pm 180^\circ$  relative to the output being fed back. So, a loop gain of  $A\beta_F = -1$  (magnitude 1, phase -180 degrees) precisely meets the oscillation condition.

## The Criterion Explained Qualitatively:

The Nyquist Stability Criterion states that:

- For a feedback system to be **stable**, the Nyquist plot of the loop gain  $A\beta_F$  must **NOT encircle the critical point (-1, 0)** in the complex plane.
- If the plot **encircles the critical point (-1, 0)**, the system is **unstable**, indicating that it will oscillate.

### Visualization:

- Imagine a path tracing the Nyquist plot as frequency increases.
- If this path passes through the point  $(-1, 0)$ , the system is on the verge of oscillation.
- If the path encloses  $(-1, 0)$  (meaning you are on one side of it as frequency approaches 0, and on the other side as frequency goes to infinity, indicating a "loop" around it), the system is unstable.
- If the path stays entirely on one side of  $(-1, 0)$ , the system is stable.

## Relationship to Bode Plots (More Practical Approach)

While the Nyquist plot offers a complete picture, generating and interpreting it precisely can be involved. For practical feedback amplifier design, **Bode plots** are far more commonly used because they provide a simpler, more intuitive way to assess stability by separating the magnitude and phase information.

A Bode plot consists of two graphs:

1. **Magnitude Plot:**  $|A\beta F|$  in decibels (dB) versus log frequency.
2. **Phase Plot:**  $\angle(A\beta F)$  in degrees versus log frequency.

The Nyquist criterion has direct implications for the Bode plots:

- **Stability Condition from Bode Plots:** A feedback amplifier operating with negative feedback is generally considered stable if:
  - When the magnitude of the loop gain  $|A\beta F|$  crosses 0 dB (the point where  $|A\beta F|=1$ ), the corresponding phase shift  $\angle(A\beta F)$  is **less than 180 degrees in magnitude** (or equivalently, less negative than -180 degrees, e.g., -150 degrees). This ensures that there is still a significant "margin" before the phase shifts enough to cause positive feedback.
  - Alternatively, when the phase shift  $\angle(A\beta F)$  reaches exactly -180 degrees, the magnitude of the loop gain  $|A\beta F|$  must be **less than 0 dB** (i.e.,  $|A\beta F|<1$ ). This ensures that even if the phase condition for oscillation is met, the gain is insufficient to sustain it.

These conditions on Bode plots are essentially simplified checks based on the comprehensive Nyquist criterion. They provide easily identifiable visual cues for stability. The concept of **Gain Margin** and **Phase Margin**, derived directly from Bode plots, quantitatively expresses how far a system is from satisfying the Barkhausen criterion, thus quantifying its stability.

---

## 5.7 Gain Margin and Phase Margin: Quantifying Stability, Importance in Design

**Gain Margin (GM)** and **Phase Margin (PM)** are quantitative metrics derived from the Bode plot of the loop gain ( $A\beta F$ ) that precisely indicate how far a feedback amplifier is from the unstable operating point. They are indispensable tools for feedback amplifier design, allowing engineers to not only confirm stability but also to gauge its robustness and predict the system's transient response.

Both margins measure the "safety distance" from the Barkhausen oscillation criteria ( $|A\beta F|\geq 1$  and  $\angle(A\beta F)=0^\circ$  or  $360^\circ$ ).

### 1. Gain Margin (GM)

- **Definition:** Gain Margin is the amount (in decibels, dB) by which the loop gain  $|A\beta F|$  can be increased *at the frequency where the phase shift is exactly 180 degrees (or*

-180 degrees) before the system becomes unstable. It tells us how much "extra" gain we have before oscillation.

- **How to Find GM on a Bode Plot:**

1. **Identify the Phase Crossover Frequency ( $\omega_{pc}$ ):** Locate the frequency on the phase plot where the phase angle of the loop gain  $\angle(A\beta F)$  crosses the -180-degree line. This is the frequency where the feedback becomes positive feedback.
2. **Read the Gain at  $\omega_{pc}$ :** At this  $\omega_{pc}$ , find the corresponding magnitude of the loop gain  $|A\beta F|$  (in dB) from the magnitude plot. Let this be  $|A\beta F|_{dB, \omega_{pc}}$ .
3. **Calculate Gain Margin:**  
 $GM = 0 \text{ dB} - |A\beta F|_{dB, \omega_{pc}}$ 
  - If the magnitude at  $\omega_{pc}$  is negative dB (i.e.,  $|A\beta F| < 1$ ), then GM will be positive, indicating a stable system.
  - If the magnitude at  $\omega_{pc}$  is positive dB (i.e.,  $|A\beta F| > 1$ ), then GM will be negative, indicating an unstable system (oscillating at  $\omega_{pc}$ ).
  - If the magnitude at  $\omega_{pc}$  is exactly 0 dB (i.e.,  $|A\beta F| = 1$ ), then  $GM = 0$  dB, meaning the system is marginally stable and on the verge of oscillation.

- **Desired Value:** A generally accepted minimum Gain Margin for good stability is around **10 to 15 dB**. This provides a safety factor against component variations and environmental changes.

**Numerical Example: Gain Margin** From a Bode plot, you identify that the loop gain phase crosses -180 degrees at a frequency of 5 MHz. At this frequency, the magnitude of the loop gain is found to be -8 dB.

Calculate the Gain Margin:  $GM = 0 \text{ dB} - (-8 \text{ dB}) = 8 \text{ dB}$

This amplifier has a positive Gain Margin of 8 dB, indicating it is stable, but relatively close to the edge of instability. For many applications, a higher margin would be preferred.

## 2. Phase Margin (PM)

- **Definition:** Phase Margin is the additional phase lag (in degrees) that can be introduced *at the frequency where the loop gain magnitude is exactly 0 dB (unity gain)* before the system becomes unstable. It tells us how much "extra" phase shift we can tolerate before oscillation.
- **How to Find PM on a Bode Plot:**
  1. **Identify the Gain Crossover Frequency ( $\omega_{gc}$ ):** Locate the frequency on the magnitude plot where the loop gain  $|A\beta F|$  crosses the 0 dB line (meaning  $|A\beta F| = 1$ ). This is the frequency at which the gain condition for oscillation is met.
  2. **Read the Phase at  $\omega_{gc}$ :** At this  $\omega_{gc}$ , find the corresponding phase angle of the loop gain  $\angle(A\beta F)$  (in degrees) from the phase plot. Let this be  $\angle(A\beta F)_{\omega_{gc}}$ .
  3. **Calculate Phase Margin:**  
 $PM = 180^\circ + \angle(A\beta F)_{\omega_{gc}}$

(Note:  $\angle(A\beta F)\omega_{gc}$  will typically be a negative angle for phase lag. For example, if it's -120 degrees, then  $PM=180^\circ+(-120^\circ)=60^\circ$ .)

- If PM is positive, the system is stable.
- If PM is negative, the system is unstable (oscillating at  $\omega_{gc}$ ).
- If PM is exactly 0 degrees, the system is marginally stable.
- **Desired Value:** A generally accepted minimum Phase Margin for good stability and desirable transient response is around **45 to 60 degrees**. A PM below 45 degrees can lead to undesirable overshoot and ringing in the amplifier's step response.

**Numerical Example: Phase Margin** From the same Bode plot, you identify that the loop gain magnitude crosses 0 dB at a frequency of 2 MHz. At this frequency, the phase angle of the loop gain is found to be -130 degrees.

Calculate the Phase Margin:  $PM=180^\circ+(-130^\circ)=50^\circ$

This amplifier has a positive Phase Margin of 50 degrees, which is generally considered good, indicating a stable system with a reasonably damped transient response.

## Importance of Gain Margin and Phase Margin in Design

GM and PM are indispensable for robust feedback amplifier design for several crucial reasons:

1. **Quantitative Stability Assessment:** They move beyond qualitative statements (stable/unstable) to provide concrete numerical values for stability. This allows engineers to compare different designs and quantify their resilience.
2. **Predicting Robustness:** Larger positive GM and PM values indicate a more robust and forgiving design. Such an amplifier can tolerate greater variations in component values (due to manufacturing tolerances, aging, or temperature changes) or changes in load characteristics without breaking into oscillation. A design with small margins is inherently fragile.
3. **Predicting Transient Response and Ringing:** Phase Margin is particularly critical for predicting the amplifier's transient response (how it reacts to sudden changes in input, like a step voltage).
  - A **low PM (e.g., 0-30 degrees)** indicates a highly underdamped system, which will likely exhibit significant **overshoot** and **ringing** (oscillations that decay slowly) in response to a step input. If PM is 0 or negative, it oscillates indefinitely.
  - A **moderate PM (e.g., 45-60 degrees)** typically represents a good compromise between fast response and minimal overshoot/ringing. This range is often targeted for general-purpose amplifiers.
  - A **high PM (e.g., > 75 degrees)** indicates a heavily damped or "sluggish" response. While very stable, the amplifier might be too slow for high-speed applications.
4. **Guiding Frequency Compensation:** If initial analysis (or prototyping) reveals insufficient GM or PM, these margins directly inform the necessary **frequency compensation** techniques. Compensation involves strategically adding components

(usually small capacitors) to modify the amplifier's frequency response characteristics.

- The goal of compensation is to deliberately introduce a dominant pole or strategically place zeros to ensure that the loop gain drops below 0 dB *before* the phase reaches -180 degrees. This increases both PM and GM, pushing the system away from the instability boundary.
- For example, if PM is too low, a compensation capacitor might be added to roll off the gain earlier, moving the gain crossover frequency to a point where the phase lag is less.